

Assignment

1. What are the Laws of Electrical circuits?
2. Explain the Earthing system and its need.
3. Write in detail about electrical wiring system and its types.
4. What are the different wiring diagrams?